



DVA494

Programming of Reliable Embedded Systems

Obed Mogaka | Hamid Mousavi | Masoud Daneshtalab

IDT, Mälardalens University

January 12, 2026

Today's Agenda

- State Diagram vs. ASM Charts.
- ASM Components
- Register Transfer Methodology
- FSM and ASMD Models.
- Deriving the ASM Chart:
 - Sequential Binary Multiplier.


State Machine (SM) Charts

- A state machine controls a digital system to carry out a step-by-step algorithm.
- **Problem:** Traditional State Diagrams ("bubbles and arcs") work well for simple logic but become cluttered and hard to read for complex algorithms.
- The **SM Chart** (or ASM Chart).
 - A special type of flowchart used to describe the behavior of a state machine.
 - "ASM" stands for **Algorithmic State Machine**.
- **Why use them?**
 - They resemble software flowcharts (intuitive).
 - They directly represent the hardware timing (Clock Cycles).
 - They serve as a blueprint for VHDL coding.

Comparison: State Diagram vs. ASM Chart

 
1. State Graph

- **Nodes:** Unique states.
- **Arcs:** Transitions labeled with conditions.
- **Drawback:** Hard to visualize complex data operations.



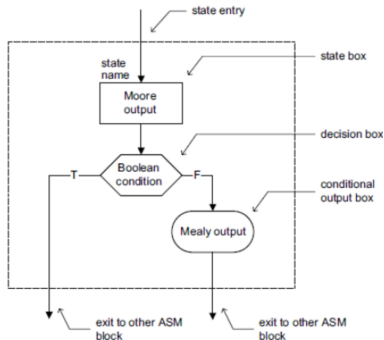
2. ASM Chart

- Composed of a network of **ASM Blocks**.
- More descriptive for applications with complex transitions and actions.




ASM Components: 1. The State Box

- **Function:** Represents a single state in the ASM/FSM.
- The state box contains a *state name* followed by a slash (/) and an optional output list.
 - A *state code* (binary encoding) may be placed above the box.
 - **Output List:** Moore-type outputs (depend only on the present state) and unconditional register-transfer operations that occur whenever the machine is in this state.
- **Timing Rule:** All actions inside the state box occur in parallel and complete within **one clock cycle**.
- Once the next clock edge arrives, the machine transitions to the next state.

 


ASM Components: 2. The Decision Box

- **Function:** Implements the control-flow decision used to select the next path in the ASM.
- The decision box is drawn as a *diamond* and represents a Boolean test.
 - Has **one entry point** and **two or more exit paths** (e.g., True/False or multi-way conditions).
 - Contains a **Boolean expression** evaluated based on the current state and input signals (e.g., `Start = '1'` or `Count = Max`).
 - Guides the transition to the appropriate next state or conditional output block.
- **Timing Rule:** The decision box is **purely combinational** and does **not** consume a clock cycle. Its output is evaluated within the same cycle as the state that precedes it.

 


ASM Components: 3. The Conditional Output Box

- **Function:** Describes **Mealy-type outputs** or operations that occur only under specific input conditions.
- The conditional output box is drawn as an *oval* (or rounded rectangle).
 - It always appears on a branch coming from a Decision Box.
 - The actions listed inside execute **only** when the Boolean condition leading to this branch is true.
 - Typical uses include: asserting control signals, enabling devices, or performing conditional register-transfer operations.
- **Timing Rule:** This box represents **pure combinational logic**. The outputs respond **immediately** to changes in the inputs and present state— no clock edge is required (asynchronous with respect to the clock).

 

Putting it Together: The ASM Block

- An ASM chart is formed by connecting multiple **ASM Blocks** in sequence.
- An **ASM Block** consists of:
 - Exactly **one State Box** (the root of the block), and
 - All **Decision Boxes** and **Conditional Output Boxes** that can be reached from that state before entering the next state.
- **Structure:**
 - The block has **one entrance path** (into the state box).
 - It may have **one or many exit paths**, each corresponding to a unique sequence of decisions and conditional outputs.
 - A complete route from entrance to an exit is called a **Link Path**.
- **Purpose:** Encapsulates all possible actions and decisions performed during the **one clock cycle** in which the machine is in that state.

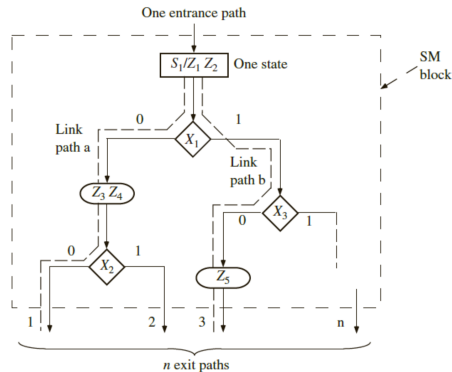

Simple Example: Rising Edge Detector as an ASM Chart

Goal: Detect a rising edge on the input signal `level`. The output `tick` becomes 1 for one clock cycle when `level` changes from 0 to 1.

State Logic (State Diagram Interpretation):


- **State zero:**

- Input `level` = 0: stay in zero.
- Input `level` = 1: - Assert `tick` = 1 (rising edge detected) - Go to **state one**.


- **State one:**

- Input `level` = 1: stay in one.
- Input `level` = 0: go back to **state zero**.

 This is a simple **Mealy machine**: the output `tick` depends on both the current state and the input (`level`).



(a) State diagram

 


(b) ASM chart


VHDL Implementation: Rising Edge Detector

Mapping ASM to VHDL:

 - The **State Box** corresponds to the `when` clause.
- The **Decision Box** becomes the `if` statement.
- The **Conditional Output** goes *inside* the `if`.



(a) State diagram

 

(b) ASM chart



```
1 architecture mealy_arch of edge_detect is
2     type state_type is (zero, one);
3     signal state_reg, state_next : state_type;
4 begin
5     -- Process 1: State Register (Sequential)
6     process(clk, reset)
7     begin
8         if reset='1' then
9             state_reg <= zero;
10        elsif rising_edge(clk) then
11            state_reg <= state_next;
12        end if;
13    end process;
14
15    -- Process 2: Next State & Output Logic
16    process(state_reg, level)
17    begin
18        state_next <= state_reg; -- Default
19        tick <= '0'; -- Default
20
21        case state_reg is
22            when zero =>
23                if level = '1' then -- Decision Box
24                    tick <= '1'; -- Conditional Output
25                    state_next <= one;
26                end if;
27            when one =>
28                if level = '0' then -- Decision Box
29                    state_next <= zero;
30                end if;
31        end case;
32    end process;
33 end mealy_arch;
```

Equivalent ASM Charts: Same Logic, Different Forms

An ASM block can be drawn in several different but **functionally equivalent** ways.

The order in which input conditions are tested may change the diagram's shape, **but not the logic it implements**.

  
- Two SM blocks may differ in:
 - order of decisions,
 - grouping of conditions,
 - placement of conditional output boxes.
- **They are equivalent if:**
 - all tests lead to the same exit paths, and
 - they generate the same outputs.
- Even combinational circuits can be expressed as ASM charts.




Rules for Constructing an SM Block

Two fundamental rules must always be followed when drawing an ASM (SM) block:

 1. **Each valid input combination must produce exactly one exit path.**
 - Ensures deterministic behavior.
 - Multiple exit paths may exist, but only one is taken per cycle.
2. **No internal feedback is allowed inside an SM block.**
 - Feedback must occur **between** SM blocks, never within.
 - Prevents multiple passes through a block in the same clock cycle.



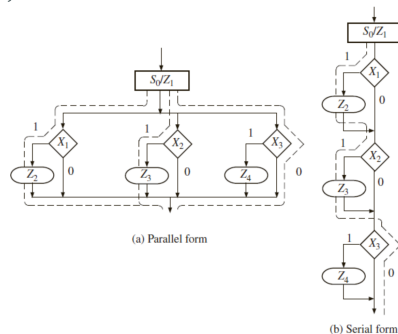
Incorrect vs. correct SM block with feedback.



Parallel vs. serial equivalent SM blocks.


From State Graph to SM Chart: The Conversion

 - The conversion process is mechanical and reversible.
- Every State Bubble becomes an **SM Block**.



- **Nodes:** S_0, S_1, S_2
- **Moore Out:** Z_a, Z_b, Z_c (Inside node)
- **Mealy Out:** Z_1, Z_2 (On arc)

Target: SM Chart

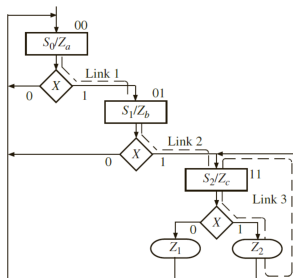


- **State Box:** Contains Moore outputs (Z_a).
- **Decision Box:** Checks inputs (X).
- **Conditional Box:** Contains Mealy outputs (Z_1).

Note: Link paths (dashed lines) show the flow of control through one clock cycle.

Register Transfer Methodology (RTM)


- **Concept:** Complex digital systems are best described by the movement and processing of data between registers.
- **Micro-operations:** Elementary operations performed on data stored in registers during one clock cycle.
 - *Transfer:* $R1 \leftarrow R2$
 - *Arithmetic:* $R1 \leftarrow R1 + R2$
 - *Logic:* $R1 \leftarrow R1 \text{ xor } R2$
 - *Shift:* $R1 \leftarrow R1 \ll 1$
- **Conditional Transfer:** Operations can be controlled by a logic condition (K).

If ($K = 1$) then ($R2 \leftarrow R1$)

 


The FSM Model (FSM + Datapath)

- To implement an algorithm, we separate the circuit into two distinct units:
- **1. The Datapath (Data Processor):**
 - Contains registers, functional units (ALUs), and routing (muxes).
 - Performs the actual data manipulation.
 - Generates **Status Signals** (flags) for the controller.
- **2. The Control Unit (Controller):**
 - An FSM that sequences the operations.
 - Generates **Control Signals** to tell the datapath what to do.

 

The ASMD Chart (ASM with Datapath)

- This is an extension of the ASM chart that incorporates Register Transfer (RT) operations directly into the boxes.
- **Key Feature:** It links the *timing* (FSM state) with the *action* (Datapath operation).
- **Syntax Update:**
 - **State Box:** Lists register updates that happen *at the next clock edge* if the machine is in this state.
 - **Conditional Box:** Lists register updates that happen *only* if the condition path is taken.

 


Deriving the ASM Chart: Sequential Binary Multiplier

Sequential Binary Multiplier – Idea and Motivation

 Problem Description:

The multiplication of two binary numbers can be done with paper and pencil by successive (i.e., sequential) additions and shifting.

- A **sequential** hardware multiplier mimics this process:
 - processes **one bit** of the multiplier per clock cycle
 - reuses a **single adder**, some registers and a shifter
 - cheaper and smaller than a fully parallel multiplier.
- **Our goal in this section:**
 - understand the algorithm,
 - design a suitable datapath,
 - derive an FSM,
 - and finally express the controller as an **ASM chart**.




From Paper-and-Pencil Multiplication to Hardware

Paper-and-pencil binary multiplication:

 1. Examine each bit of the multiplier, starting from the **LSB**.
2. If the bit is 1, add a suitably shifted copy of the multiplicand to the partial sum.
3. Shift and move to the next bit.

Sequential hardware will:

- inspect **one multiplier bit per clock cycle**,
- optionally perform an **add**, then a **shift**,
- repeat these steps until all bits have been processed.




Sequential Binary Multiplier – Interface

External interface:

- Inputs:
 - **A** (multiplicand), **B** (multiplier)
 - **S** (start) – begins a new multiplication
 - **Reset** – clears the internal state
- Output:
 - **P** – final product (up to $2n$ bits for n -bit operands)

Architecture overview:

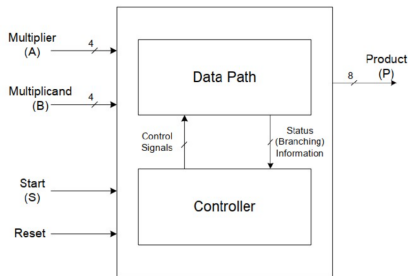- **Datapath** performs all arithmetic and shifting.
- **Controller** is an FSM that:
 - sequences the operations in time,
 - generates the datapath **control signals**,
 - receives **status signals** (e.g., LSB, counter zero) from the datapath.



Sequential Binary Multiplication – Algorithm

Informal pseudocode for n -bit operands:

Algorithm 1 Sequential Binary Multiplication

Require: Two n -bit binary numbers: A (multiplicand) and B (multiplier)

Ensure: $P = A \times B$

```
1:  $P \leftarrow 0$                                 initial product
2: for  $i \leftarrow 0$  to  $n - 1$  do
3:   if  $B[i] = 1$  then
4:      $P \leftarrow P + (A \ll i)$               add shifted multiplicand
5:   end if
6: end for
7: return  $P$ 
```


Observation:

- The loop body processes **one bit** of the multiplier.
- In hardware we will:
 - avoid shifting A by i in one step,
 - instead shift the *partial product* and multiplier registers by 1 each cycle.

Multiplier Datapath – Registers and Units

Key registers:

- **B-register** (multiplicand):
 - Stores B for the entire operation.
- **P-register** (partial product):
 - Split into P_H and P_L .
 - Initially: $P_H = 0$, $P_L = A$ (multiplier).
 - Final product is (E, P_H, P_L) .
- **E-register:**
 - 1-bit register for the adder carry-out,
 - behaves as the MSB of the product.
- **Cnt:**
 - down-counter initialised to n ,
 - determines when all multiplier bits are processed.

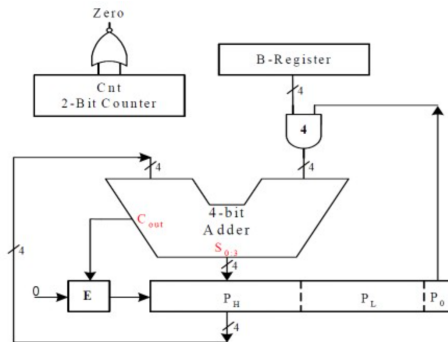


Datapath Operation – One Iteration

Per clock cycle (iteration):

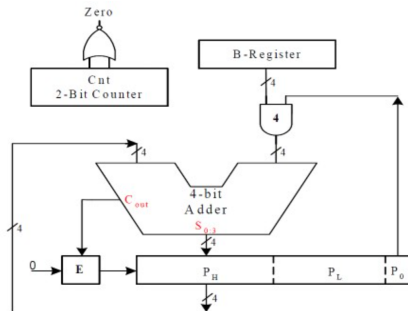1. Look at the least significant bit of P_L (the current multiplier bit).
2. **If that bit is 1:**
 - add B to P_H using the adder,
 - store sum in P_H and carry-out in E .
3. **Shift** the concatenated register (E, P_H, P_L) one bit to the right.
4. **Decrement** the counter.
5. If the counter is not zero, repeat from step 1 on the next cycle.

Important:

- The multiplicand B never changes.
- The multiplier bits are *consumed* as P_L shifts right.
- After n iterations, (E, P_H, P_L) holds the final $2n$ -bit product.



Example Walkthrough (Conceptual)

Consider $A = 1011_2$, $B = 1101_2$ (4-bit example).

Initial state:

- $P_H = 0000$, $P_L = A = 1011$, $E = 0$
- $\text{Cnt} = 4$

For each cycle:

1. Check LSB of P_L :
 - if 1 \Rightarrow add B into P_H ,
 - if 0 \Rightarrow skip the addition.
2. Shift (E, P_H, P_L) right by one bit.
3. Decrement Cnt .

After 4 cycles:

- $\text{Cnt} = 0$ and (E, P_H, P_L) equals the product $A \times B$.
- This cycle-by-cycle behaviour is exactly what our FSM will control.

Datapath Control Signals

Load and clear operations:


- **Clr_PH** – clear the upper half of the product.
- **Ld_PL** – load the multiplier into P_L .
- **Ld_B** – load the multiplicand into the B-register.
- **Ld_Cnt** – load the loop counter with n .

Runtime operations:

- **Ld_PH** – load adder sum into P_H .
- **Ld_E** – load adder carry-out into E .
- **Shift_Rt** – shift (E, P_H, P_L) right by one bit.
- **Dec_Cnt** – decrement counter by 1.

Status (branching) signals back to controller:

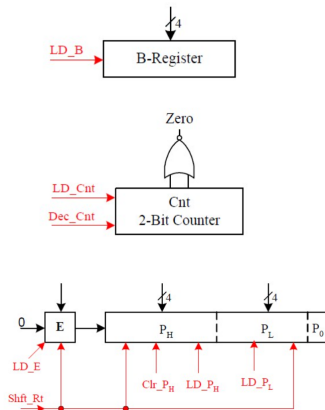
- P_0 – current LSB of P_L (multiplier bit).
- **Zero** – counter has reached zero.




Multiplier Controller – FSM

States (informal meaning):

 - S_0 (Idle/Init):
 - wait for Start,
 - when asserted: load datapath registers and counter.
- S_1 (Test/Add):
 - inspect LSB of P_L ,
 - if $P_0=1$: perform addition.
- S_2 (Shift/Loop):
 - shift and decrement counter,
 - if counter $\neq 0$: go back to S_1 ,
 - otherwise: go to **Done**.
- **Done (optional state or flag):**
 - product is ready at (E, P_H, P_L) .




ASM Chart for the Sequential Multiplier

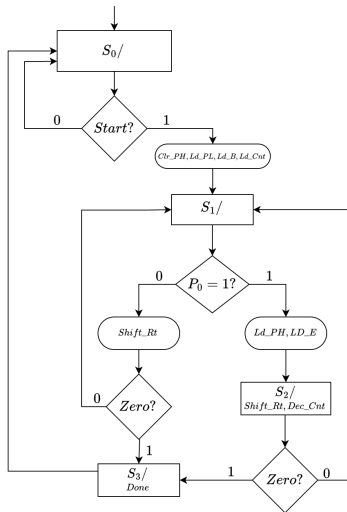

The ASM Chart (Controller)

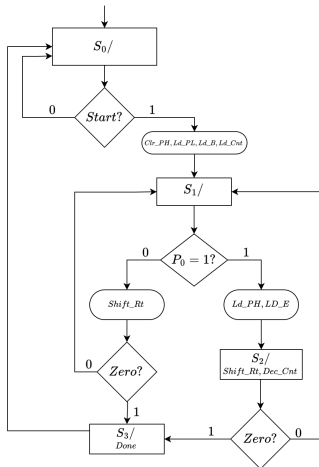The controller sequences the operations based on the Multiplier bit (`P0`) and the Counter status (`Zero?`).



State Walkthrough:

- **So (Idle):** Waits for `Start`. If 1, loads all registers (`Ld_B`, `Ld_PL`, etc.).
- **S1 (Test/Process):** Checks LSB of Multiplier (`P0`).
 - **If 1 (Add needed):** Triggers Add (`Ld_PH`) and moves to **S2** to shift later.
 - **If 0 (No Add):** Shifts immediately (`Shift_Rt`). Checks Counter (`Zero?`). If done, go to **S3**; else loop back to **S1**.
- **S2 (Shift):** Only entered after an Add. Performs the Shift and Decrement. Checks `Zero?` to decide loop termination.
- **S3 (Done):** Asserts `Done` flag. Returns to **So**.

VHDL Implementation: The Controller (FSM)

The controller acts as the brain, sequencing operations based on status flags (`start` , `zero_flag`) and driving datapath control signals.

1. State Register & Transitions

```
1  -- FSM State Register (Sequential)
2  process (clk, resetn)
3  begin
4      if resetn = '0' then
5          state <= S0;
6      elsif rising_edge(clk) then
7          state <= next_state;
8      end if;
9  end process;
10
11  -- Next State Logic (Combinational)
12  process (state, start, zero_flag)
13  begin
14      case state is
15          when S0 => -- Idle
16              if start = '1' then next_state <= S1;
17              else next_state <= S0; end if;
18
19          when S1 => -- Load / Setup
20              if start = '0' then next_state <= S2;
21              else next_state <= S1; end if;
22
23          when S2 => -- Shift / Compute
24              if zero_flag = '0' then next_state <= S1; -- Loop
25              else next_state <= S0; end if; -- Done
26
27          when others => next_state <= S0;
28      end case;
29  end process;
```

2. Output Logic (Datapath Control)

```
1  -- Output Logic (Combinational)
2  process (state, start)
3  begin
4      -- Default values (prevent latches)
5      load_PH <= '0'; load_PL <= '0'; load_E <= '0';
6      load_Cnt <= '0'; shift_Rt <= '0'; clr_PH <= '0';
7      dec_Cnt <= '0'; load_B <= '0';
8
9      case state is
10         when S0 => -- Initialization
11             if start = '1' then
12                 clr_PH <= '1';
13                 load_PL <= '1';
14                 load_B <= '1';
15                 load_Cnt <= '1';
16             end if;
17
18         when S1 => -- Prepare for Op
19             if start = '0' then
20                 load_PH <= '1'; -- Add/Load
21                 load_E <= '1';
22             end if;
23
24         when S2 => -- Shift & Count
25             shift_Rt <= '1';
26             dec_Cnt <= '1';
27
28         end case;
29  end process;
```

Summary: From Algorithm to ASM to VHDL

- Began with the **manual** binary multiplication procedure.
- Derived a structured **pseudocode** algorithm.
- Designed a **datapath** with registers, adder, shifter, counter.
- Identified the necessary **control signals** and status signals.
- Built an **FSM** that sequences:
 - initialisation,
 - conditional add,
 - shift/decrement and loop,
 - termination.
- Expressed the FSM as an **ASM chart**:
 - one state box per clock cycle,
 - decision boxes for PLO and Zero,
 - conditional output box for Mealy-style add operation.

This approach generalises: *start from the algorithm, define the datapath, design the FSM, and finally capture it as an ASM chart.*