



DVA494

Programming of Reliable Embedded Systems

Obed Mogaka | Hamid Mousavi | Masoud Daneshtalab

IDT, Mälardalens University

January 18, 2026

Review of Logic Design Fundamentals

- Boolean Algebra and Algebraic Simplification
- Karnaugh Maps
- Designing With NAND and NOR Gates
- Combinational Logic
- Hazards in Combinational Circuits

How Computers/Digital/Embedded Systems Work!

How Computers/Digital/Embedded Systems Work!
How Can We Design a Digital System!

Why Do We Do Computing?

Why Do We Do Computing?

To Solve Problems, Gain Insight, and Enable a Better Life and Future.

Why Do We Do Computing?

To Solve Problems, Gain Insight, and Enable a Better Life and Future.

- **How Does a Computer Solve Problems?**

Why Do We Do Computing?

To Solve Problems, Gain Insight, and Enable a Better Life and Future.

- **How Does a Computer Solve Problems?** Orchestrating Electrons

Why Do We Do Computing?

To Solve Problems, Gain Insight, and Enable a Better Life and Future.

- **How Does a Computer Solve Problems?** Orchestrating Electrons
- **How Do Problems Get Solved by Electrons?**

Why Do We Do Computing?

To Solve Problems, Gain Insight, and Enable a Better Life and Future.

- **How Does a Computer Solve Problems?** Orchestrating Electrons
- **How Do Problems Get Solved by Electrons?** I don't know

The Art of Managing Complexity

- Abstraction
- Discipline
- The Three-Y's
 - Hierarchy
 - Modularity
 - Regularity

Hiding details when they are not important

| Abstraction Levels | Examples |
|-----------------------------|-------------------------|
| Application Software | Programs |
| Operating Systems | Device drivers |
| Architecture | Instructions, Registers |
| Micro architecture | Datapath, Controllers |
| Logic | Adders, Memories |
| Digital Circuits | AND gates, NOT gates |
| Analog Circuits | Amplifiers |
| Devices | Transistors, Diodes |
| Physics | Electrons |

Discipline: Intentionally restricting your design choices to that you can work more productively at higher abstraction levels.


- **Digital Discipline:** We consider only two discrete values: 1's and 0's.
 - How Much Can We Do with 1s and 0s?

The Three-Y's

- Hierarchy
 - A system is divided into modules of smaller complexity
- Modularity
 - Having well defined functions and interfaces
- Regularity
 - Encouraging uniformity, so modules can be easily re-used

The Transformation Hierarchy

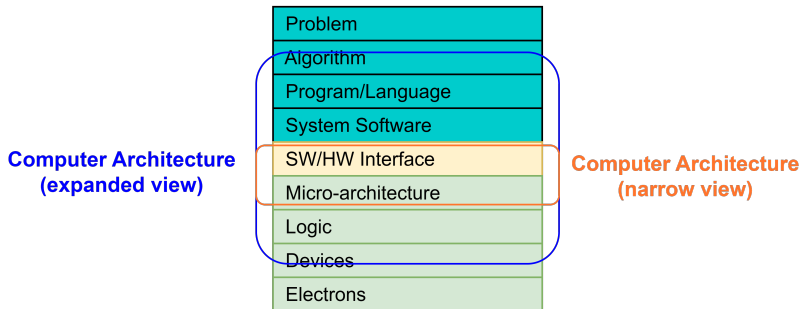We are in the Logic and Microarchitecture section.



The core of computer architecture:


designing, selecting, and **interconnecting** hardware components and the hardware/software interface to create a computing system that meets **functional, performance, energy consumption, cost,** and other specific goals.

Why is it so Important Today?

- Performance , Energy Efficiency, Sustainability
- **Reliability**, Safety, Security, Privacy
- New (Device) Technologies

Logic Gates and Boolean Algebra

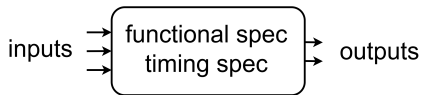A logic circuit is composed of: inputs and outputs.




- Functional specification (describes relationship between inputs and outputs)
- Timing specification (describes the delay between inputs changing and outputs responding)

Basic Logic Gates

They implement simple Boolean functions:

Buffer

 

| A | Z |
|---|---|
| 0 | 0 |
| 1 | 0 |

AND



| A | B | Z |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

OR



| A | B | Z |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

XOR



| A | B | Z |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Inverter



| A | Z |
|---|---|
| 0 | 1 |
| 1 | 0 |

NAND



| A | B | Z |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

NOR



| A | B | Z |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

XNOR




| A | B | Z |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Functional Specification

- Functional Specification can be specified by a truth table.
- **Truth Table:** A tabular listing of function values for all possible combinations of values on its input arguments.
- Truth table is the unique signature of a Boolean function but, it is an expensive representation.
- If there are n inputs, there are 2^n possible combinations.
- A Boolean function can have many alternative Boolean expressions.
- i.e., many alternative Boolean expressions (and gate realizations) may have the same truth table (and function).
- If they all specify the same thing, why do we care? Different Boolean expressions lead to different logic gate implementations → **different cost, latency, and energy properties.**
- **Canonical form:** standard form for a Boolean expression provides a unique algebraic signature.

Two-Level Canonical (Standard) Forms

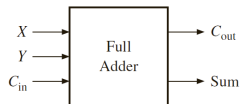Derive algebraic expressions for Sum and C_{out} from the truth table of a Full Adder:



(a) Full adder module

| X | Y | C_{in} | C_{out} | Sum |
|-----|-----|----------|-----------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

(b) Truth table

- Sum and C_{out} can be formed by ORing the **minterms** together.

$$Sum = \bar{X}\bar{Y}C_{in} + \bar{X}Y\bar{C}_{in} + X\bar{Y}\bar{C}_{in} + XYC_{in}$$


$$C_{out} = \bar{X}YC_{in} + X\bar{Y}C_{in} + XY\bar{C}_{in} + XYC_{in}$$

- These are **Sum of Products (SOP)** expressions.
- They can also be expressed as:

$$Sum = m_1 + m_2 + m_4 + m_7 = \sum m(1, 2, 4, 7)$$

$$C_{out} = m_3 + m_5 + m_6 + m_7 = \sum m(3, 5, 6, 7)$$

Two-Level Canonical (Standard) Forms

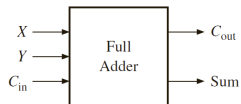

(a) Full adder module

| X | Y | C_{in} | C_{out} | Sum |
|-----|-----|----------|-----------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

(b) Truth table

- Sum and C_{out} can also be formed by ANDing the **maxterms**.

$$Sum = (X + Y + C_{in})(X + \bar{Y} + \bar{C}_{in})(\bar{X} + Y + \bar{C}_{in})(\bar{X} + \bar{Y} + C_{in})$$

$$C_{out} = (X + Y + C_{in})(X + Y + \bar{C}_{in})(X + \bar{Y} + C_{in})(\bar{X} + Y + C_{in})$$

- These are **Product of Sums (POS)** expressions.
- They can also be expressed as:

$$Sum = M_0 \cdot M_3 \cdot M_5 \cdot M_6 = \prod M(0, 3, 5, 6)$$

$$C_{out} = M_0 \cdot M_1 \cdot M_2 \cdot M_4 = \prod M(0, 1, 2, 4)$$

Using Boolean Equations to Represent a Logic Circuits

Boolean equations enable us to do the following:

- Represent the function of a combinational logic block (Functional Specification)
- Methodically transform the function into simpler functions
 - which lead to different hardware realizations
 - Logic Minimization or Logic Simplification
 - We can automate this process Computer-Aided Design or Electronic Design Automation
 - Different Boolean expressions lead to different logic gate implementations → Different hardware area, cost, latency, energy properties

Boolean Algebra and Algebraic Simplification

The basic mathematics used for logic design is Boolean algebra.

Summary of the laws and theorems of Boolean algebra:

| | |
|------------------------|---|
| Variable dominant rule | $X \cdot 1 = X, X + 0 = X$ |
| Commutative rule | $X \cdot Y = Y \cdot X, X + Y = Y + X$ |
| Complement rule | $X \cdot \bar{X} = 0, X + \bar{X} = 1$ |
| Idempotency | $X \cdot X = X, X + X = X$ |
| Identity Element | $X \cdot 0 = 0, X + 1 = 1$ |
| Double negation | $\bar{\bar{X}} = X$ |
| Associative rule | $X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z, X + (Y + Z) = (X + Y) + Z$ |
| Distributive rule | $X \cdot (Y + Z) = X \cdot Y + X \cdot Z, X + Y \cdot Z = (X + Y)(X + Z)$ |
| Absorption | $X \cdot (X + Y) = X \cdot X + X \cdot Y = X$ $X + X \cdot Y = X \cdot (1 + Y) = X$ |
| Adjacency | $X \cdot Y + X \cdot \bar{Y} = X$ $(X + Y)(X + \bar{Y}) = X$ |
| Consensus | $X \cdot Y + \bar{X} \cdot Z + Y \cdot Z = X \cdot Y + \bar{X} \cdot Z$ $(X + Y)(\bar{X} + Z)(Y + Z) = (X + Y)(\bar{X} + Z)$ <i>Corollary:</i> $(X + Y)(\bar{X} + Z) = \bar{X} \cdot Y + X \cdot Z$ |
| DeMorgan | $X \cdot Y = \overline{\bar{X} + \bar{Y}}$ $X + Y = \overline{\bar{X} \cdot \bar{Y}}$ |
| Simplification | $X \cdot (\bar{X} + Y) = X \cdot Y$ $X + \bar{X} \cdot Y = X + Y$ |

Algebraic Simplifications

Four ways of simplifying a logic expression using the theorems are as follows:

1. Combining terms.
2. Eliminating terms.
3. Eliminating literals.
4. Adding redundant terms.

Practice! Practice!

Simplification Examples

Example 1:

$$F = (A + \overline{B}C + D + EF)(A + \overline{B}C + \overline{D + EF})$$

Example 2:

$$F = \overline{(\overline{X + Y})Z + (X\overline{Y}Z)}$$

Simplification Examples

Example 1:

$$F = (A + \bar{B}C + D + EF)(A + \bar{B}C + \overline{D + EF})$$

$$F = (X + Y)(X + \bar{Y}),$$

$$\text{where } X = A + \bar{B}C, Y = D + EF$$

$$F = (X + Y)(X + \bar{Y}) = X$$

$$\rightarrow F = X = A + \bar{B}C$$

Example 2:

$$F = \overline{(\overline{X + Y})Z + (X\bar{Y}Z)}$$

Simplification Examples

Example 1:

$$F = (A + \bar{B}C + D + EF)(A + \bar{B}C + \overline{D + EF})$$

$$F = (X + Y)(X + \bar{Y}),$$

$$\text{where } X = A + \bar{B}C, Y = D + EF$$

$$F = (X + Y)(X + \bar{Y}) = X$$

$$\rightarrow F = X = A + \bar{B}C$$

Example 2:

$$F = \overline{(\bar{X} + Y)Z + (X\bar{Y}Z)}$$

$$F = \overline{\bar{X}\bar{Y}Z + X\bar{Y}Z}$$

$$F = \overline{\bar{Y}Z(X + \bar{X})}$$

$$\rightarrow F = \overline{\bar{Y}Z} = Y + \bar{Z}$$

Simplification Examples

Example 3:

$$F = x_1x_2 + \overline{x_1x_2} + x_2\overline{x_1}$$

Example 4:

$$F = \overline{A(B + \overline{C}) + \overline{A}}$$

Simplification Examples

Example 3:

$$F = x_1x_2 + \overline{x_1x_2} + x_2\overline{x_1}$$

$$F = x_1x_2 + \overline{x_1}(x_2 + \overline{x_2}) = x_1x_2 + \overline{x_1}$$

$$F = \overline{x_1} + x_1x_2 = (\overline{x_1} + x_1)(\overline{x_1} + x_2)$$

$$\rightarrow F = \overline{x_1} + x_2$$

Example 4:

$$F = \overline{A(B + \overline{C}) + \overline{A}}$$

Simplification Examples

Example 3:

$$F = x_1x_2 + \overline{x_1x_2} + x_2\overline{x_1}$$

$$F = x_1x_2 + \overline{x_1}(x_2 + \overline{x_2}) = x_1x_2 + \overline{x_1}$$

$$\begin{aligned} F &= \overline{x_1} + x_1x_2 = (\overline{x_1} + x_1)(\overline{x_1} + x_2) \\ &\rightarrow F = \overline{x_1} + x_2 \end{aligned}$$

Example 4:


$$F = \overline{A(B + \overline{C})} + \overline{A}$$

$$\begin{aligned} F &= \overline{A(B + \overline{C})}.A = (\overline{A} + \overline{B + \overline{C}}).A \\ &\rightarrow F = \overline{(B + \overline{C})}.A = A\overline{B}C \end{aligned}$$

Deriving Circuits Functions from Truth Tables


| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |
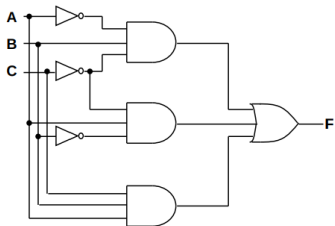
$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC$$



| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |
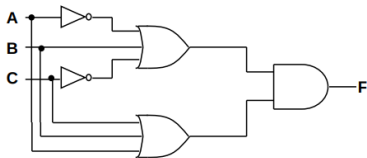
$$F = (A + B + C)(\bar{A} + B + \bar{C})$$



Logic Simplification using Karnaugh Maps (K-Maps)

- Karnaugh Map (K-map) method K-map is an alternative method of representing the truth table that helps visualize adjacencies in up to 6 dimensions.
- Physical adjacency means Logical adjacency

| <i>A</i> \ <i>B</i> | 0 | 1 |
|---------------------|----|----|
| 0 | 00 | 01 |
| 1 | 10 | 11 |

3-Variable K-Map

| <i>A</i> \ <i>BC</i> | 00 | 01 | 11 | 10 |
|----------------------|-----|-----|-----|-----|
| 0 | 000 | 001 | 011 | 010 |
| 1 | 100 | 101 | 111 | 110 |


4-Variable K-Map

| <i>AB</i> \ <i>CD</i> | 00 | 01 | 11 | 10 |
|-----------------------|------|------|------|------|
| 00 | 0000 | 0001 | 0011 | 0010 |
| 01 | 0100 | 0101 | 0111 | 0110 |
| 11 | 1100 | 1101 | 1111 | 1110 |
| 10 | 1000 | 1001 | 1011 | 1010 |


Two- and Three-Variable Karnaugh Maps

Two-variable K-Map:

 - Minterms in adjacent squares of the map can be combined since they differ in only one variable.
- Thus, $\overline{A}B$ and $\overline{A}\overline{B}$ combine to form \overline{A} , and this is indicated by looping the corresponding 1's on the map in (d)




Three-variable K-Map:

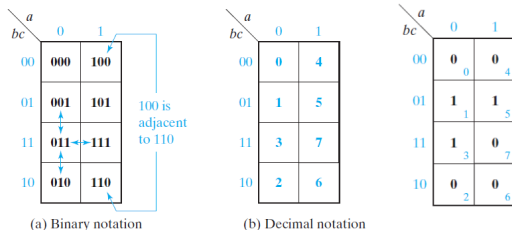

Three-Variable Karnaugh Maps


 
Simplification of a Three-Variable Function




Three-Variable Karnaugh Maps

Location of Minterms on Four-Variable Karnaugh Map and Simplification of functions


| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| | 0 | 4 | 12 | 8 |
| 00 | 0 | 4 | 12 | 8 |
| 01 | 1 | 5 | 13 | 9 |
| 11 | 3 | 7 | 15 | 11 |
| 10 | 2 | 6 | 14 | 10 |

 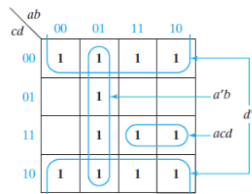

(a)

 


(b)



 


Determination of Minimum Expressions Using Essential Prime Implicants

- In choosing adjacent squares in a map, we must ensure that:
 - All the minterms of the function are covered when we combine the squares
 - The number of terms in the expression is minimized
 - There are no redundant terms (i.e., minterms already covered by other terms)
- A **prime implicant** is a product term obtained by combining the maximum possible number of adjacent squares in the map.
- If a minterm in a square is covered by only one prime implicant, that prime implicant is said to be **essential**.

 


  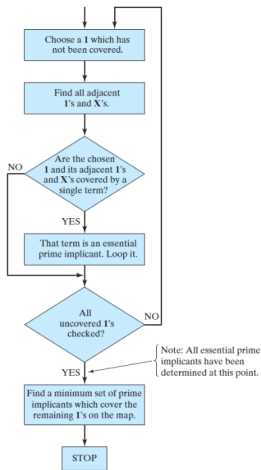Determination of Minimum Expressions Using Essential Prime Implicants



$$f = CD + BD + B'C + AC$$

(a)

 

$$f = BD + B'C + AC$$

(b)

NOTE: Simplification using K-Maps is limited. When the number of variables is large or if several functions must be simplified the computer-based **Quine-McCluskey** method is used.

Designing With NAND and NOR Gates

- In many technologies, implementation of **NAND** gates or **NOR** gates is easier than that of AND and OR gates.
- The bubble at a gate input or output indicates a complement.
- Any logic function can be realized using only NAND gates or only NOR gates.

NAND:




NOR:




Gate Delays and Timing Diagrams

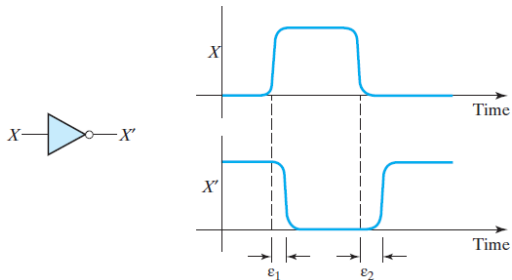- When the input to a logic gate is changed, the output will not change instantaneously.
- The transistors or other switching elements within the gate take a finite time to react to a change in input-
propagation delay.



Timing Diagrams

Timing Diagram for Circuit with Delay

 

Hazard: An unintended output glitch in a combinational circuit caused by unequal path propagation delays when inputs change:

- **Static-1 hazard:** Output momentarily falls to 0 when it should remain 1.
- **Static-0 hazard:** Output momentarily rises to 1 when it should remain 0.
- **Dynamic hazard:** During an intended $0 \rightarrow 1$ or $1 \rightarrow 0$ change, the output toggles multiple times (three or more) before settling.


Hazards in Combinational Circuits




(a) Simple circuit with static 1-hazard




(b) Simple circuit with static 0-hazard

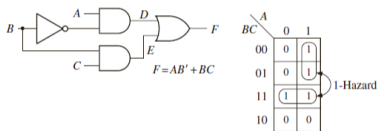

(a) Circuit with 1-hazard

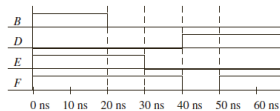

(b) Timing chart

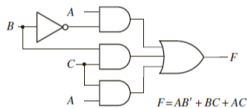

(c) Circuit with hazard removed

| | | | | |
|----|---|---|---|--|
| | A | 0 | 1 | |
| BC | 0 | 1 | | |
| 00 | 0 | 1 | | |
| 01 | 0 | 1 | | |
| 11 | 1 | 1 | | |
| 10 | 0 | 0 | | |

Combinational Logic

- **Combinational Logic**

- Memoryless
- Outputs are strictly dependent on the combination of input values that are being applied to circuit right now


- **Sequential Logic**

- Has memory - Can "store" data values
- Outputs are determined by previous (historical) and current values of inputs

Multiplexers


Multiplexers: act as data routing switches, needed in many applications.

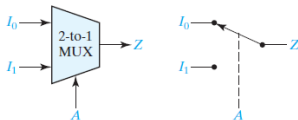2-to-1 Multiplexer and Switch Analog $Z = A'I_0 + AI_1$





Multiplexers
 
$$Z = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3$$




Implementation of an 8-to-1 MUX.

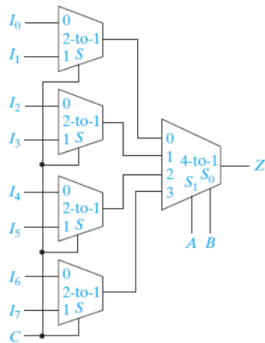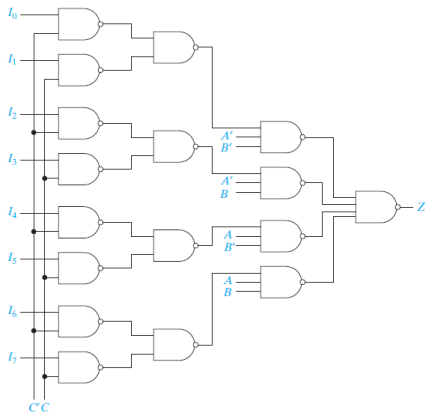

Three State Buffers

 
- A gate output can only be connected to a limited number of other device inputs without degrading the performance of a digital system.
- A simple buffer may be used to increase the driving capability of a gate output.



| <i>B</i> | <i>A</i> | <i>C</i> | <i>B</i> | <i>A</i> | <i>C</i> | <i>B</i> | <i>A</i> | <i>C</i> | <i>B</i> | <i>A</i> | <i>C</i> |
|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|
| 0 | 0 | Z | 0 | 0 | Z | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | Z | 0 | 1 | Z | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | Z | 1 | 0 | Z |
| 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | Z | 1 | 1 | Z |



(a) (b) (c) (d)

Data Selection Using Three-State Buffers

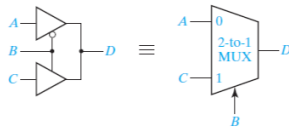


Decoders and Encoders

  Consider a **A 3-to-8 Line Decoder**: it generates all of the minterms of the three input variables.



(a) Logic diagram

 

(b) Block diagram

| BCD Input | | | | Decimal Output | | | | | | | | | |
|-----------|---|---|---|----------------|---|---|---|---|---|---|---|---|---|
| A | B | C | D | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 |
| 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

(c) Truth Table

Review the following cases:

- Full-adder
- Carry-ripple adder
- Faster adders:
 - Manchester
 - Carry-lookahead
 - Kogge-stone tree
- Adder arrays
- Parallel multiplier
- Comparators (equality and greater-than/equal-to)
- Arithmetic logic unit (ALU)



Half Adder

Half Adder

| x | y | C | S |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

$$S = x'y + xy'$$


$$C = xy$$

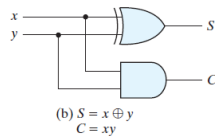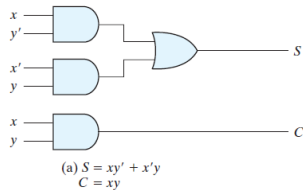


Full Adder

Full Adder

| x | y | z | C | S |
|-----|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |



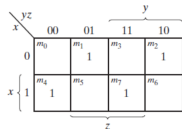


$$(a) S = x'y'z + x'yz' + xy'z' + xyz$$

 

$$(b) C = xy + xz + yz$$

   
$$\begin{aligned}
 S &= z \oplus (x \oplus y) \\
 &= z'(xy' + x'y) + z(xy' + x'y)' \quad C = z(xy' + x'y) + xy = xy'z + x'yz + xy \\
 &= z'(xy' + x'y) + z(xy + x'y') \\
 &= xy'z' + x'yz' + xyz + x'y'z
 \end{aligned}$$



Binary Adder-Subtractor


A binary adder produces the arithmetic sum of two binary numbers.

 It can be constructed with full adders connected in cascade



| Subscript i : | 3 | 2 | 1 | 0 | |
|-----------------|---|---|---|---|-----------|
| Input carry | 0 | 1 | 1 | 0 | C_i |
| Augend | 1 | 0 | 1 | 1 | A_i |
| Addend | 0 | 0 | 1 | 1 | B_i |
| Sum | 1 | 1 | 1 | 0 | S_i |
| Output carry | 0 | 0 | 1 | 1 | C_{i+1} |

 
The subtraction of unsigned binary numbers can be done most conveniently by means of complements subtraction $A - B$ can be done by taking the 2's complement of B and adding it to A .



Arithmetic Logic Unit

ALU circuits are at the core of any microprocessor or microcontroller.

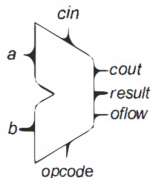Its capable of computing several logic as well as arithmetic functions.



(a)

(b)

| Unit | opcode | Instruction | result |
|------------|--------|--------------------------------------|----------------------------------|
| Logic | 0000 | Complement <i>a</i> | not <i>a</i> |
| | 0001 | Complement <i>b</i> | not <i>b</i> |
| | 0010 | Logic and | <i>a</i> and <i>b</i> |
| | 0011 | Logic or | <i>a</i> or <i>b</i> |
| | 0100 | Logic nand | <i>a</i> nand <i>b</i> |
| | 0101 | Logic nor | <i>a</i> nor <i>b</i> |
| | 0110 | Logic xor | <i>a</i> xor <i>b</i> |
| | 0111 | Logic xnor | <i>a</i> xnor <i>b</i> |
| Arithmetic | 1000 | Transfer <i>a</i> | <i>a</i> |
| | 1001 | Transfer <i>b</i> | <i>b</i> |
| | 1010 | Increment <i>a</i> | <i>a</i> + 1 |
| | 1011 | Increment <i>b</i> | <i>b</i> + 1 |
| | 1100 | Decrement <i>a</i> | <i>a</i> - 1 |
| | 1101 | Decrement <i>b</i> | <i>b</i> - 1 |
| | 1110 | Add <i>a</i> and <i>b</i> | <i>a</i> + <i>b</i> |
| | 1111 | Add <i>a</i> and <i>b</i> with carry | <i>a</i> + <i>b</i> + <i>cin</i> |

See you next time!